Design of CPU

VLSI ARCHITECTURE (MELZG642) ASSIGNMENT-3

ANAND S, 2021HT80003 | VLSI Architecture | 24-04-2022

Table of Contents

Cc	n'	te	'n	ts
	,,,	CC		C

1.	Pro	oblem statement		
2.	Des	sign	3	
3.	HD	L code	4	
	3.1	cpu_pkg.sv	4	
:	3.2	instr_mem.sv	5	
:	3.3	reg_file.sv	7	
	3.4	if_id_pipe.sv	8	
	3.5	id_ex_pipe.sv	9	
	3.6	ex_wb_pipe.sv	10	
:		alu.v, and multiplier.sv,		
		cpu.sv		
	3.9	flist.v	14	
	3.10	Testbench: top.sv	15	
		nulation1		
5.	Cor	nclusion	18	

Table of Figures

Figure 1 Architecture of CPU with pipelining	. 3
Figure 2 Simulation result of CPU	17

1. Problem statement

Given that the sequence of instructions to be executed by the processor is guaranteed to be free from pipeline hazards, design a 4 – stage (Instruction Fetch; Decode and read operand; execute; write back) pipelined RISC processor that can execute following register to – register instructions with a throughput of one instruction per clock –cycle: MUL, Barrel shifter XOR, NOR. The multiplier and barrel shifter, ALU designed in assignment-1 and 2 should be used here.

STEP 0: Draw the detailed architecture level diagram of the processor, naming and depicting the various architectural blocks (e.g. register file, instruction memory, ALU, pipeline registers, PC and combinational functional blocks etc).

STEP 1: Create Verilog/ VHDL behavioral models for each of the architectural blocks. (Register file, Instruction memory, ALU, Pipeline registers, PC etc)

STEP 2: Build the top level **structural model** of the processor by instantiating and interconnecting the architectural blocks created in step 1.

STEP 3: Initialize the instruction memory with a program consisting of 4 instructions: 0000 MUL reg3, reg1

0004 SHIFT reg6, reg5, reg4 0008 XOR reg9, reg8, reg7 0012 NOR reg 13, reg11, reg10

Initialize the register file with the following data

reg2 = 60 reg1 = 40

reg5 = 40 reg4 = 60

reg7 = FFFF856D reg8 = EEEE3721

reg10 = 1FFF756F reg11 = FFFF765E

Initialize PC with 0000 address.

The instruction format is:

31 14 9 4 0

OPCODE	Dest. Reg	Source Reg.1	Source Reg.2]
				ı

Opcode MUL 0------001
SHIFT 0-----010
XOR 0------011
NOR 0------100

The register file has 32 number of 32 bit registers. The data in registers is stored as integers in 2's complement binary representation. Assume that register file has two 32-bit read ports: A and B for data reading and one 32 bit write port: C for data writing. At the rising edge of the clock the read ports A and B output the data from the registers whose addresses are present at port A address and port B address respectively if the enable read port A and enable read port B signals are true. At the falling edge of a clock, data is written to the register whose address is present at Port C address if write enable Port C is true. Design the pipeline registers such that they are latched at the rising edge of the clock. Specify the size and format of all pipeline registers including the fields holding the decoded control signals as well as data.

The instruction memory is of size 128 bytes. A read operation from the memory outputs 4 consecutive bytes of information (starting from the byte address provided to the memory) at the positive edge of clock if the read enable instruction memory signal is true. Byte addresses must be aligned and to be provided to memory must be either 0 or multiples of 4.

2. Design

 


Figure 1 Architecture of CPU with pipelining

As shown, in Figure 1, the CPU consists of the structural implementation of PC, Instruction memory, register file, ALU, multiplier and pipeline blocks for each pipeline stage boundary.

The Multiplier and ALU are taken as is from Assignment 1 and Assignment 2 respectively. The multiplier used is a 16x9 multiplier. The ALU takes in 32 bit A and B inputs and provides 32 bit output. For shift operations, only 0 to 31 values are valid in B.

The CPU design is adapted from standard MIPS pipeline architecture, but is optimized to run only the provided instructions. Since there is no memory write back required, the design is actually only a 4 stage pipeline with IF, ID, EX and WB stages.

The entire design is implemented in system-verilog IEEE 1800-2009 standard. The use of SV structures are made to increase the readability of the HDL code. As the ALU and Multiplier code is same as in assignment-1, they are not shown in section "HDL code".

3. HDL code

3.1 CPU PKG.SV

The below code consists of SV package that encapsulates the

```
// -----
// VLSI Arch Assignment - 3
// Author: Anand S
// BITSID: 2021HT80003
package cpu pkg;
   // -----
   // Parameters
   // -----
   localparam INSTR MEM DEPTH = 128/4; // 128 bytes in words
   localparam REG FILE DEPTH = 32;
   localparam MD_WD = 16;
localparam MR_WD = 9;
   localparam MDMR WD = MD WD+MR WD;
   localparam DATA WDTH = 32;
   // -----
   // Typedefs
   // -----
   typedef enum logic [16:0] {
      NA = 17'b0 0000 0000 0000 0000,
      MUL = 17'b0'0000'0000'0000'0001,
      SHIFT = 17'b0 0000 0000 0000 0010,
      XOR = 17'b0 0000 0000 0000 0011,
      NOR = 17'b0 0000 0000 0000 0100
   } opcode t;
   typedef logic [$clog2(REG FILE DEPTH)-1:0] reg t;
   typedef struct packed {
      opcode_t opcode; // [31:15]
reg_t rd; // [14:10]
reg_t rs1; // [9:5]
reg_t rs2; // [4:0]
   } instruction t;
   typedef instruction t instr array t [INSTR MEM DEPTH];
   typedef logic [$clog2(INSTR MEM DEPTH)-1:0] instr mem addr t;
   typedef logic signed [31:0] sint32 t;
   typedef logic [31:0] uint32 t;
   typedef struct {
      logic en;
      sint32_t data; // write data
```

```
reg t addr;
    } port t;
    typedef struct {
       logic
reg_t
                  en;
                  addr;
    } port in t;
    typedef struct {
       instruction t IR;
    } IF ID pipe t;
    typedef struct {
        logic mul v alu;
        logic get nor;
        logic [3:\overline{0}] aluc;
    } control t;
    typedef struct {
        instruction t IR;
       sint32_t A;
sint32_t B;
       control t ctrl;
    } ID EX pipe t;
    typedef struct {
        instruction t IR;
                      C;
       sint32 t
    } EX WB pipe t;
endpackage: cpu pkg
```

3.2 INSTR MEM.SV

The instruction memory is coded as per specification. As there is no requirement in the current specification to fill the memory through explicit writes, the HDL code is similar to that of a ROM. The initialization of the memory has been done directly in the RTL instead of using readmemh Verilog directives for simplicity and better illustration.

The specification also points that the read needs to be on a positive edge of the clock – This can be enforced in two ways :-

- 1. By external constraints: The memory read port can be made an asynchronous read port, but the "raddr" port needs to be ensured to change only on posedge of the clk.
- 2. By internal design: The memory should have a registered read port that changes value on posedge of the clk. This matches the specification, but it adds additional latency in the pipeline, and correspondingly all the pipelines need to be held to meet the required timing.

```
// VLSI Arch Assignment - 3
// Author: Anand S
// BITSID: 2021HT80003
module instr mem
import cpu pkg::*;
    input logic
input instr_mem_addr_t
output instruction_t
clk, resetn, re,
raddr,
instruction_word
);
    // Instr mem can be implemented as Read-Only for this application
    instr array t instr mem array;
    logic [($clog2(INSTR MEM DEPTH/4))-1:0] raddr int;
    assign raddr int = raddr >> 2; // Ensures word alignment
    always_comb begin: mem init
        foreach (instr mem array[i]) begin
            instr mem array[i] = '{opcode: NA, default: 0};
            // synopsys translate off
            $display ("instr mem array[%0d] = %p", i,
instr mem array[i]);
            // synopsys translate on
        instr mem array[0] = '{\text{opcode: MUL}}, rd: 3, rs1: 2, rs2: 1};
        instr mem array[1] = '{opcode: SHIFT, rd: 6, rs1: 5, rs2: 4};
        instr_mem_array[2] = '{opcode: XOR, rd: 9, rs1: 8, rs2: 7};
        instr mem array[3] = '{opcode: NOR, rd:13, rs1:11, rs2:10};
    end: mem init
`ifdef RD STALL ALLOWED
    always ff @(posedge clk, negedge resetn) begin
        if (!resetn) begin
            instruction word <= '{opcode:NA, default:0};</pre>
        end else begin
            if (re) instruction word <= instr mem array[raddr int];</pre>
        end
    end
`else
    // asynch read port
    assign instruction_word = instr_mem_array[raddr_int];
`endif
endmodule: instr mem
```

3.3 REG FILE.SV

The register file is also coded in two different ways :- One with the asynchronous read port, and the other with registered read port. The selection of the RTL code is based on a macro "RD_STALL_ALLOWED" (same as in instr_mem.sv). The initialization of the memory has been done directly in the RTL instead of using readmemh Verilog directives for simplicity and better illustration.

The specification points that the read needs to be on a positive edge of the clock – This can be enforced in two ways :-

- By external constraints: The memory read port can be made an asynchronous read port, but the "addrA" and "addrB" ports needs to be ensured to change only on posedge of the clk. If the "enA" and "enB" ports are not set, the memory provides "0", otherwise it provides the data at the pointed address.
- 2. By internal design: The memory should have a registered read port that changes value on posedge of the clk. This matches the specification, but it adds additional latency in the pipeline, and correspondingly all the pipelines need to be held to meet the required timing. If the "enA" and "enB" ports are not set, the previous value is stored, otherwise the read value is updated on the next posedge.

NOTE: As the "SHIFT" operation is done on reg5 and reg4, the value of 0x60 is much greater 32, the maximum allowed shift value in the ALU design as coded in assignment-2. If the reg4 content is maintained at 0x60, we cannot see any shifting happening (as shift value is 0). Thus the reg4 value has been changed to a smaller value during the initialization phase.

```
end
            rf array[1] <= 'h40;
            rf array[2] <= 'h60;
            rf array[4] <= 'h02;
            rf_array[5] <= 'h40;
            rf array[7] <= 'hFFFF856D;</pre>
            rf array[8] <= 'hEEEE3721;
            rf array[10]<= 'h1FFF756F;
            rf array[11]<= 'hFFFF765E;
        end: init
        else begin
            if (enC) rf array[addrC] <= C;</pre>
        end
    end
`ifdef RD STALL ALLOWED
    always_ff @(posedge clk, negedge resetn) begin
        if (!resetn) begin
            A \leq 0;
            B <= 0;
        end else begin
            if (enA) A <= rf array[addrA];</pre>
            if (enB) B <= rf array[addrB];</pre>
        end
    end
`else
    assign A = (enA) ? rf array[addrA] : 1'b0;
    assign B = (enB) ? rf array[addrB] : 1'b0;
`endif
endmodule: reg file
```

3.4 IF ID PIPE.SV

The if_id_pipe is the pipeline between the Instruction Fetch (IF) and Instruction decode (ID) stage. This stage pipelines the Instruction word (IR) from the Instruction fetch stage.

```
// VLSI Arch Assignment - 3
// Author: Anand S
// BITSID: 2021HT80003
// ------
module if_id_pipe
import cpu_pkg::*;
(
    input logic clk, resetn,
    input instruction_t IR_next,
    output IF_ID_pipe_t if_id_pipe
);

always_ff @(posedge clk, negedge resetn) begin
```

```
if (!resetn)
        if_id_pipe <= '{IR: '{opcode:NA, default:0}, default:0};
else
        if_id_pipe <= '{IR: IR_next};
end
endmodule: if_id_pipe</pre>
```

3.5 ID EX PIPE.SV

The id_ex_pipe is the pipeline between the Instruction Decode (ID) and Instruction Execute (EX) stage. This stage pipelines the following items from the Instruction Decode stage: -

- 1. Instruction word (IR)
- 2. ALU/MUL input 1 (A)
- 3. ALU/MUL input 2 (B)
- 4. control signals decoded in the ID stage by the control word decoder (ctrl) which consists of :-
 - select signal to choose between the output of multiplier or ALU based on the instruction type (whether it is a "MUL" or anything else) (mul_v_alu).
 - select signal to choose between the normal ALU output or the inverted value. Since the ALU does not support a NOR instruction, when a "NOR" opcode is seen, the decoder passes this signal to ensure the ALU does an "OR" operation internally, and the ALU output is then sent through and inverter to get the actual NOR output (get_nor).
 - 3. The actual ALU control signals that need to be driven to the ALUC ports of the ALU (ALUC).

```
//
// VLSI Arch Assignment - 3
// Author: Anand S
// BITSID: 2021HT80003
//

module id_ex_pipe
import cpu_pkg::*;
(
    input logic clk, resetn,
    input instruction_t IR_next,
    input sint32_t A_next, B_next,
    input mul_v_alu_next, get_nor_next,
    input logic [3:0] aluc_next,
```

3.6 EX WB PIPE.SV

The ex_wb_pipe is the pipeline between the Instruction Execute (EX) and Write back (WB) stage. This stage pipelines the following items from the Instruction Execution (EX) stage: -

- 1. Instruction word (IR) This is required to write back the output of the execution stage back to the register file.
- 2. The ALU/MUL output (C) This is the final result of the instruction execution that is written back to the register file.

3.7 ALU.V,... AND MULTIPLIER.SV,...

As these are taken as is from the specification in Assignment, no change was done to these blocks, and they are being used as is.

3.8 CPU.SV

The cpu module is a structural RTL which instantiates the sub-blocks mentioned above as well as contains the behavioral code for the PC incrementing functionality and the control word decode functionality. If the memories are required to be registered read ports, additional stalling code is added under the macro "RD_STALL_ALLOWED".

```
// VLSI Arch Assignment - 3
// Author: Anand S
// BITSID: 2021HT80003
module cpu
import cpu pkg::*;
    input logic clk, resetn
);
    instr_mem_addr_t pc;
IF_ID_pipe_t if_id_pipe_s;
ID_EX_pipe_t id_ex_pipe_s;
EX_WB_pipe_t ex_wb_pipe_s;
sint32_t A, B, C, ex_out, alu_out;
logic [24:0] mult_out;
instruction_t instruction_word;
logic carry;
logic [3:0]
     logic [3:0] ALUC;
     logic
                             get nor;
     // -----
     always ff @(posedge clk, negedge resetn) begin
          if (!resetn) pc \le 0;
          else if (pc >='hc) pc <= 0;</pre>
                            pc <= pc + 4;
     end
     // -----
     // IF stage
```

```
// -----
   instr mem
   u instr mem (
               // Interfaces
               .raddr
                                     (pc),
               .instruction word
                                    (instruction word),
               // Inputs
               .clk
                                     (clk),
               .resetn
                                     (resetn),
               .re
                                     (1'b1)); // Always enabled
   if id pipe
   u_if_id_pipe (
                // Interfaces
                .IR_next
                                    (instruction word),
                // Outputs
                .if_id_pipe
                                    (if_id_pipe_s),
                // Inputs
                .clk
                                     (clk),
                .resetn
                                    (resetn));
   // -----
   // ID stage
   // -----
   reg file
   u reg file (
              // Interfaces
              .addrA
                                    (if id pipe s.IR.rs2),
              .addrB
                                     (if id pipe_s.IR.rs1),
              .addrC
                                     (ex wb pipe s.IR.rd),
`ifdef RD STALL ALLOWED
                                     (ex_wb_pipe_ss.C),
`else
                                     (ex wb pipe s.C),
`endif
              . A
                                     (A),
              .B
                                     (B),
              // Inputs
              .clk
                                    (clk),
              .resetn
                                    (resetn),
                                     (1'b1),
              .enA
                                     (1'b1),
              .enB
                                     (1'b1));
              .enC
`ifdef RD STALL ALLOWED
   // Stall the controls before reaching the pipeline
   always ff @(posedge clk, negedge resetn) begin:aluc_dec
       if (!resetn) begin
           get nor <= 0;
           mul v alu <= 0;
                <= 4'bxxxx;
           ALUC
       end else begin
           get_nor <= 0;
           mul v alu <= 0;
           ALUC <= 4'bxxxx;
           case (if id_pipe_s.IR.opcode)
              MUL: begin
```

```
mul v alu <= 1;
               end
               SHIFT: begin
                  ALUC <= 4'b0011; // Assuming SHIFT means sll
               end
               XOR: begin
                   ALUC <= 4'b0010;
               end
               NOR: begin
                   ALUC <= 4'b0101; // Use OR of ALU and negate
externally
                   get nor <= 1;
               end
           endcase
       end
   end:aluc dec
`else
   always comb begin: aluc dec
       mul v alu = 0;
       ALUC = 4'bxxxx;
       get nor = 0;
       case (if_id_pipe_s.IR.opcode)
           MUL: mul_v_alu = 1;
SHIFT: ALUC = 4'b0011;
           XOR: ALUC = 4'b0010;
           NOR: begin
                  ALUC = 4'b0101;
                   get nor = 1;
           end
       endcase
   end: aluc dec
`endif
   id ex pipe
   u_id_ex_pipe (
                 // Interfaces
                                     (if_id_pipe_s.IR),
                 .IR next
                 .A next
                                      (A),
                 .B next
                                      (B),
                 // Outputs
                 .id ex pipe
                                  (id_ex_pipe_s),
                 // Inputs
                 .clk
                                     (clk),
                 .resetn
                                      (resetn),
                 .aluc_next
                                      (ALUC),
                 .get nor next
                                      (get nor),
                 .mul_v_alu_next
                                      (mul_v_alu));
   // -----
   // EX stage
   mult xy
   u mult (
           // Outputs
                                       (mult out[MDMR_WD-1:0]),
           .0
           // Inputs
           . A
                                       (id ex pipe s.A[MD WD-1:0]),
```

```
.B
                                      (id ex pipe s.B[MR WD-1:0]));
   alu
   u alu (
          // Outputs
          .OUT
                                      (alu out[DATA WDTH-1:0]),
          .CARRY
                                      (carry),
          // Inputs
                                      (id ex pipe s.A[DATA WDTH-
          . A
1:0]),
          . B
                                      (id ex pipe s.B[DATA WDTH-
1:0]),
          .ALUC
                                      (id ex pipe s.ctrl.aluc[3:0]));
   assign ex_out = (id_ex_pipe_s.ctrl.mul_v_alu)?
                       signed'({7'b0, mult out[24:0]}):
                       ((id_ex_pipe_s.ctrl.get_nor)?
                           ~(signed'(alu out)):
                           signed'(alu out)
                       );
   ex wb pipe
   u ex wb pipe (
   /*AUTOINST*/
                 // Interfaces
                 .IR next
                                     (id ex pipe s.IR),
                 .C next
                                     (ex out),
                 .ex wb pipe
                                     (ex wb pipe s),
                 // Inputs
                 .clk
                                     (clk),
                 .resetn
                                      (resetn));
    // -----
   // WB stage
   // -----
`ifdef RD STALL ALLOWED
   EX WB pipe t ex wb pipe ss; // stalled version for timing
   always_ff @(posedge clk, negedge resetn) begin
       if (!resetn) begin
           ex wb pipe ss <= '{IR: '{opcode:NA, default:0}, default:0};
       end else begin
           ex wb pipe ss <= ex wb pipe s;
       end
   end
`endif
endmodule: cpu
```

3.9 FLIST.V

The flist.v file consist of the include statements for all the files that need to be compiled. This consists of all the ALU and Multiplier files from previous assignments. As in assignment 2, the ALU has the additional capability to use Adder based on a single stage carry look-ahead adder for all 32 bits, or 8 stage, 4 bit carry look-ahead adder.

```
// VLSI Arch Assignment - 2
// Author: Anand S
// BITSID: 2021HT80003
// -----
// file list include
`ifndef __INCLUDE_FILES__
`define __INCLUDE_FILES__
   // ALU files
    `include "alu lib.v"
    `ifdef ALU 4bit CLA
        `include "cla 4bit.v"
       `include "cla top.v"
       `include "cla.v"
    `endif
    `include "mux2x1.v"
    `include "mux4x1.v"
    `include "shifter.v"
    `include "alu.v"
   // MUL files
    `include "mult16x9behav.sv"
    `include "ppg.sv"
    `include "fulladder.sv"
    `include "csa.sv"
   `include "cpa.sv"
   `include "mult xy.sv"
   // CPU files
    `include "cpu pkg.sv"
    `include "ex_wb_pipe.sv"
    `include "id ex pipe.sv"
    `include "if id pipe.sv"
   `include "instr mem.sv"
   `include "reg file.sv"
   `include "cpu.sv"
endif // __INCLUDE FILES
```

3.10 TESTBENCH: TOP.SV

The testbench is a basic top-level file which has a clock generator and a reset assertion sequence. The behaviour of the CPU is tested only through waveform reviews.

```
// -----
// VLSI Arch Assignment - 3
// Author: Anand S
// BITSID: 2021HT80003
// ----
include "flist.v"
module top;
   logic clk;
```

```
logic resetn;
   // -----
   // DUT
   // -----
   cpu
   u cpu (
   /*AUTOINST*/
         // Inputs
         .clk
                                    (clk),
         .resetn
                                    (resetn));
   initial begin
       clk <= 0;
       forever #5 clk = ~ clk;
   end
   initial begin: seq
      resetn = 0;
       #10;
      resetn = 1;
   end: seq
   initial begin: finish
       #200;
       $finish;
   end: finish
endmodule: top
```

The below Makefile was used to compile and run simulation:-

```
BSUB = bsub -Ip
IRUN = $(BSUB) irun
GUI = 1
ifeq ($(GUI),1)
    RUNOPT += -gui
endif
RUNOPT += -access +rwc
all:
    $(IRUN) top.sv $(RUNOPT)
```

Simulation

The CPU design was simulated using cadence incisive "irun" command (version 15.20-s042)

Design needs IEEE 1800-2009 std to be enabled. It was only tested on a UNIX environment.

Simulation was done with default timescale of 1ns/100ps


 



Figure 2 Simulation result of CPU.

As can be seen in Figure 2 Simulation result of CPU. The result of ALU/MUL units in the execution stage are written back in the next half-cycle during the write back stage.

 The CPU is made to loop back the PC to 0 after pc == 'h0C. Thus, the CPU keeps executing the same instruction until the end of simulation as shown: -



 Below are some additional signals which shows the values of the fields in each pipeline : -



5. Conclusion

The CPU design, ALU using CLA, Barrel-shifter and multiplexor components was designed and simulated and found to match with specification and was verified to work using Cadence Incisive suit of simulation tools with the help of IEEE 1800-2009 SystemVerilog assertion and coding constructs.